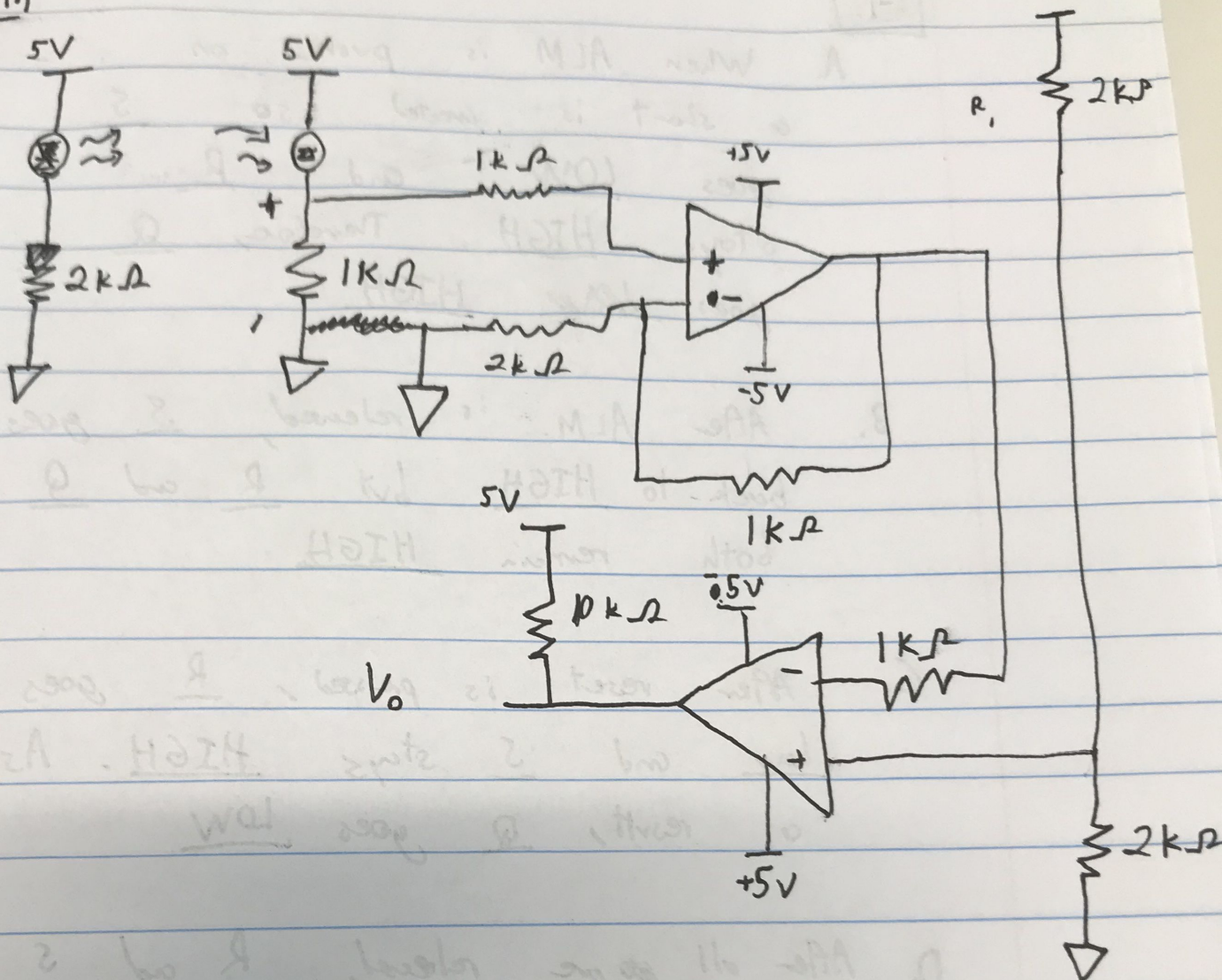


Prelab 5

A.



B.

Detector was simulated using a current source. From lab 1, $400 \mu A$ is what the detector measures with full ~~zero~~ contact and $100 \mu A$ is the substrate current. Below are the results

from SPICE

0	5V
$100 \mu A$	5V

C.

A. When ALM is pushed on
a start is created so S
goes LOW and R
stays HIGH. Therefore, Q
goes ~~LOW~~ HIGH

B. After ALM is released, S goes
back to HIGH but R and Q
both remain HIGH.

C. After reset is pressed, R goes
LOW and S stays HIGH. As
a result, Q goes LOW

D. After all are released, R and S
return HIGH and Q stays
LOW

D. When $V_B = 0$, The Green LED is on
When $V_B = 5$, The Red LED is on

To limit current to 10mA Let

$$R_g = \frac{5}{.01} = 500 \Omega$$


$$R_r = 500 \Omega$$

```

--- Operating Point ---


```

.op

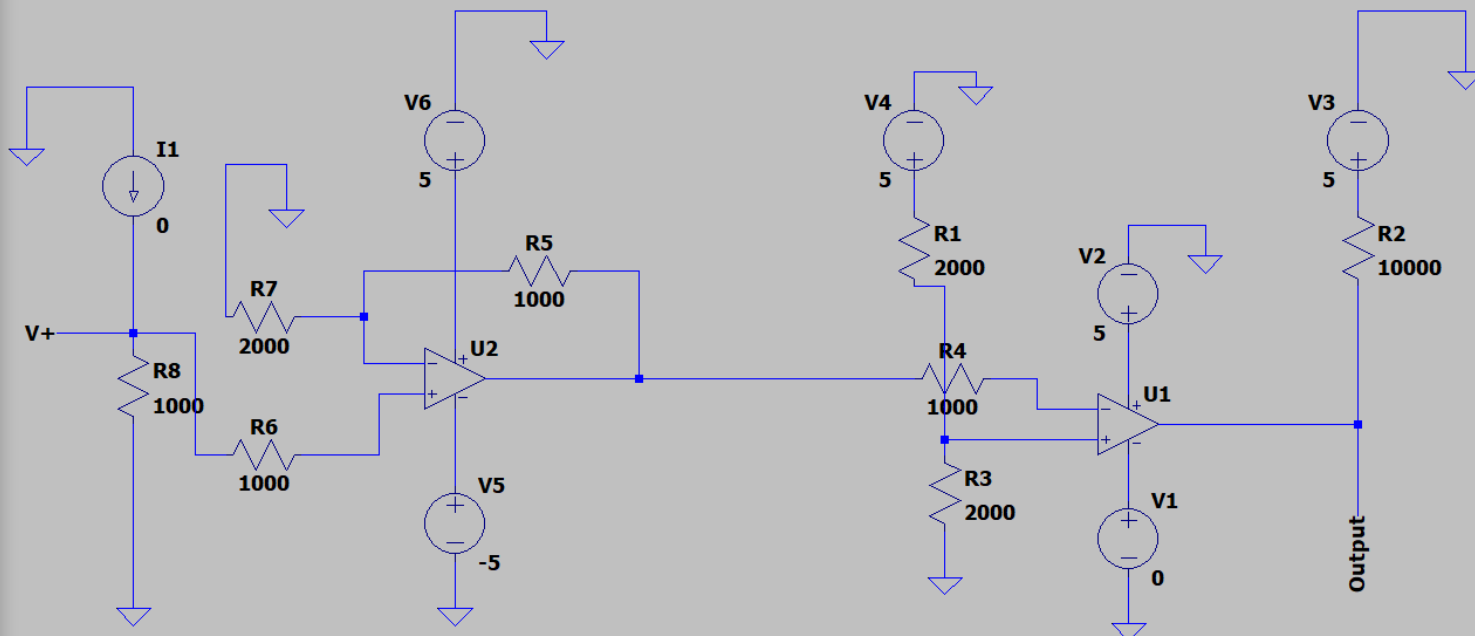

< >



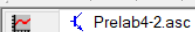


```

--- Operating Point ---

```

< >

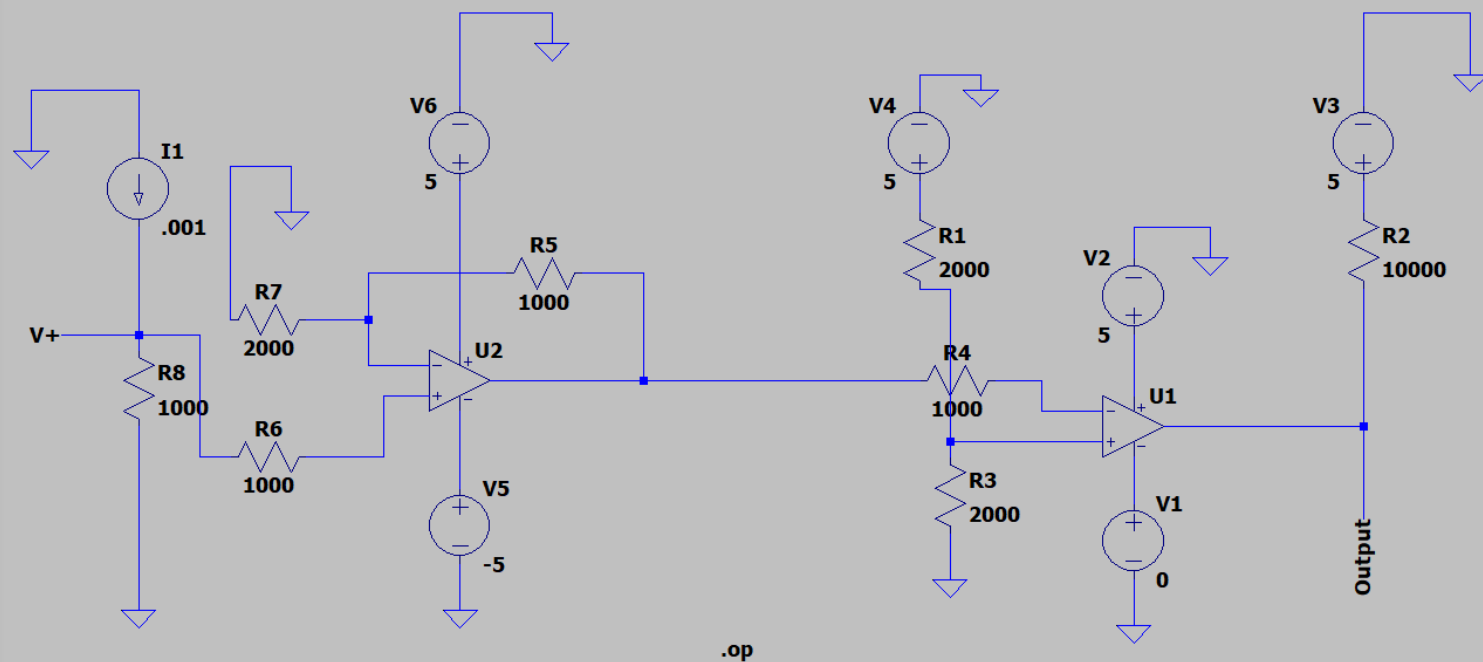

Type here to search